

ECE113 Basic Electronics Assignment 1

- 1) All Questions are compulsory.
- 2) Please use notations appropriately.
- 3) Maximum Marks:20 (4 marks each)
- 4) All the students are requested to submit hard copies of their assignments as per the deadline.
- 5) You can deposit your assignments in the respective boxes for each section (read the overleaf on each box carefully) kept near the Academic Section 2nd Floor A-wing - Old Academic Building. Please note
 - a) You must staple the assignment properly.
 - b) Mention your Name, Roll no, Section and Group clearly on each sheet of the assignment. Specify sheet number on the top of each sheet.
 - c) Use A4 size sheets only (ruled or blank). Do not submit notebooks/notepads.

——Questions——

1. Find the power absorbed by each of the elements in the circuit shown below.

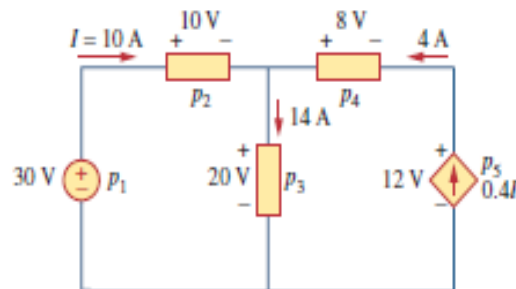


Figure 1:

2. The current through an element and voltage across it is shown below in Figure 2.
- Sketch the power delivered to the element for $t > 0$.
 - Find the total energy absorbed by the element for the period $0 < t < 4\text{s}$.

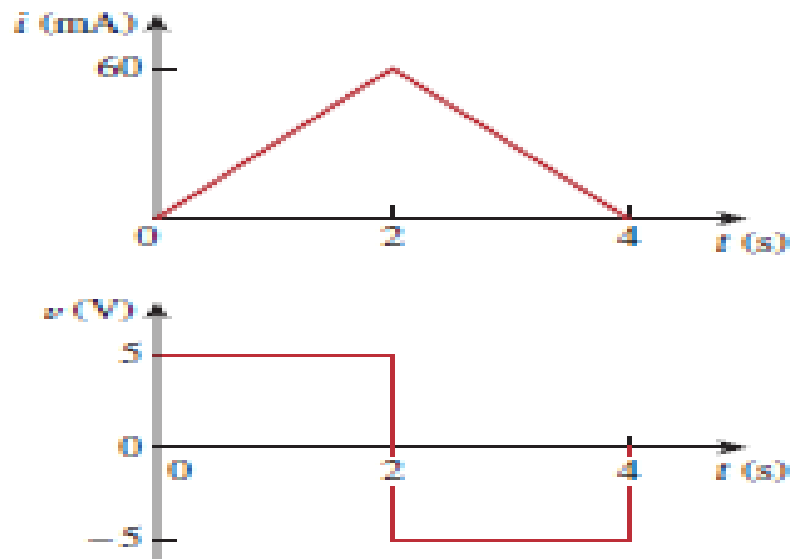


Figure 2.

3. Determine the current ' i ' and voltage ' V_o ' in the circuit shown below.

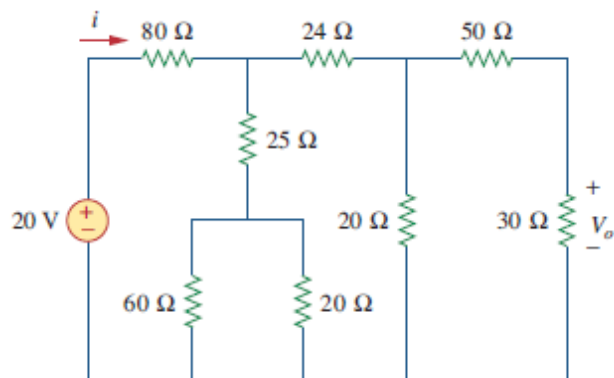


Figure 3:

4. Determine the current i_o and equivalent resistance R_{eq} for the circuit shown in Figure 4.

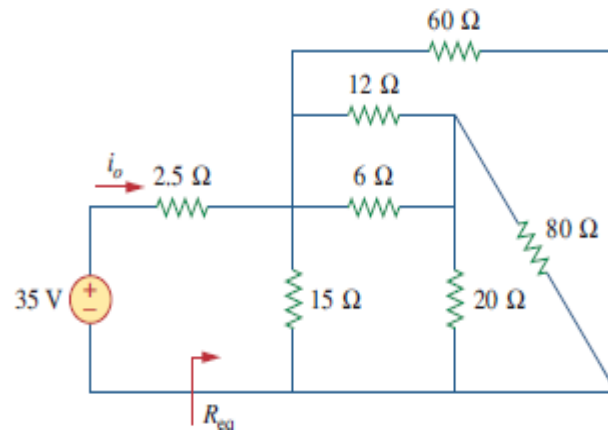


Figure 4:

5. Write the node-voltage equation and find the values of V_1 and V_2 in the given circuit.

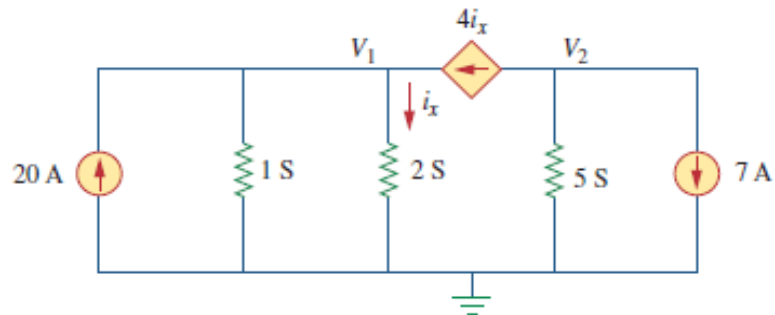


Figure 5: