

ECE113 Basic Electronics Assignment 2

- 1) All Questions are compulsory.
- 2) Please use notations appropriately.
- 3) Maximum Marks:20 (4 marks each)
- 4) All the students are requested to submit hard copies of their assignments as per the deadline.
- 5) You can deposit your assignments in the respective boxes for each section (read the overleaf on each box carefully) kept near the Academic Section 2nd Floor A-wing - Old Academic Building.
Please note
 - a) You must staple the assignment properly.
 - b) Mention your Name, Roll no, Section and Group clearly on each sheet of the assignment. Specify sheet number on the top of each sheet.
 - c) Use A4 size sheets only (ruled or blank). Do not submit notebooks/notepads.

—•—Questions—•—

1. Find the Norton equivalent at terminals a-b of the circuit shown in figure below.

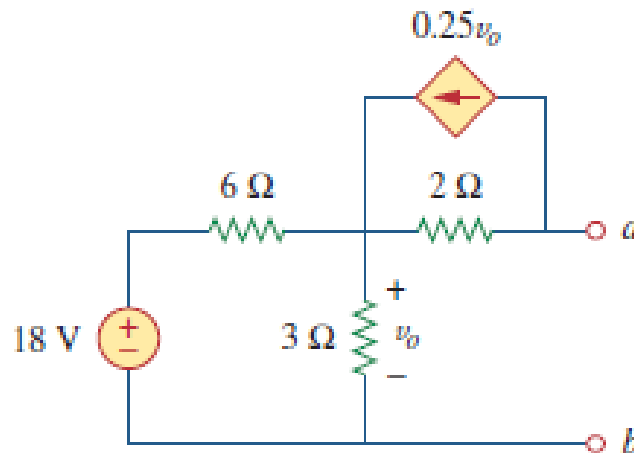


Figure 1:

2. For the circuit shown in figure below, what resistor to be connected across terminals a-b that will absorb maximum power from the circuit? What will be that power?

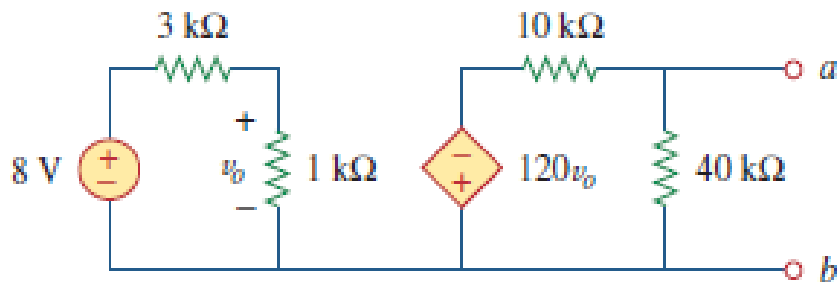


Figure 2.

3. Consider the circuit given below, determine

(a) $i_C(0^-)$, (b) $i_L(0^-)$, (c) $i_R(0^-)$, (d) $v_C(0^-)$, (e) $i_C(0^+)$, (f) $i_L(0^+)$, (g) $i_R(0^+)$, and (h) $v_C(0^+)$.

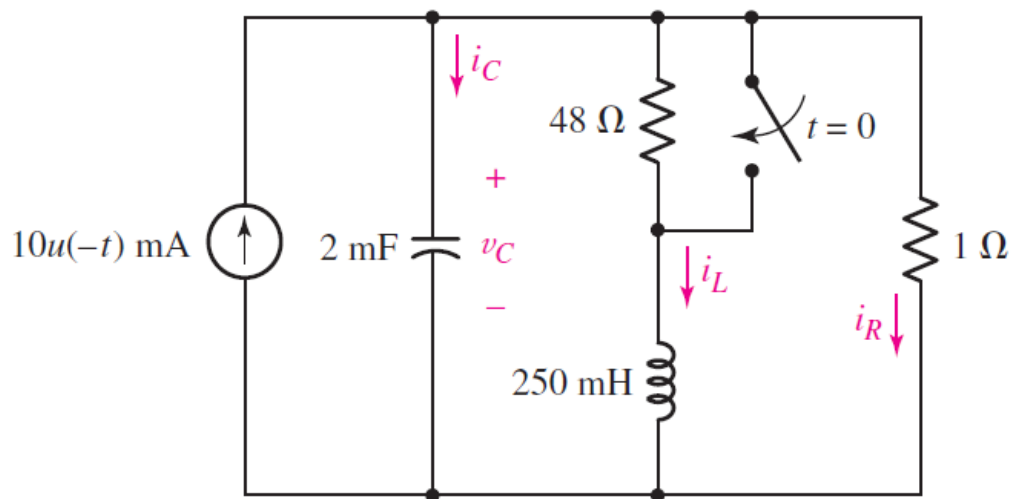


Figure 3:

4. Consider the circuit given below, the two resistor values are $R_1 = 0.752$ ohms and $R_2 = 1.268$ ohms, respectively. Obtain an expression for the energy stored in the capacitor, valid for all $t > 0$

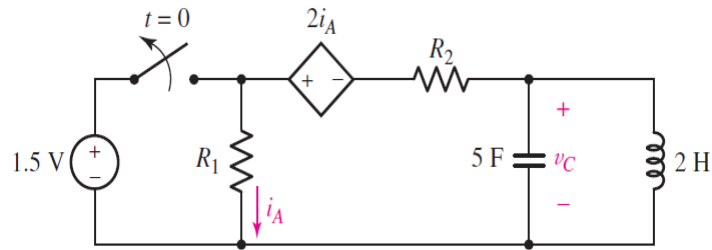


Figure 4:

5. After being open for a day, the switch in the circuit of figure below is closed at $t=0$. Find the differential equation describing $i(t)$, $t > 0$.

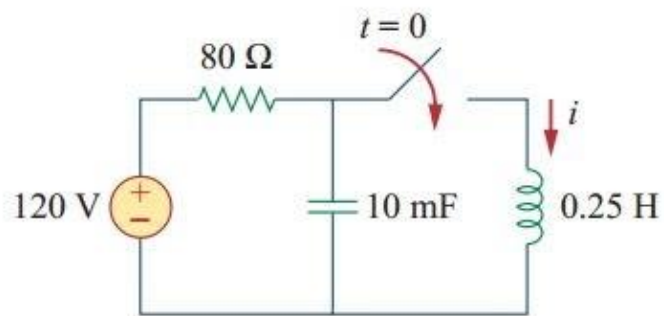


Figure 5: