
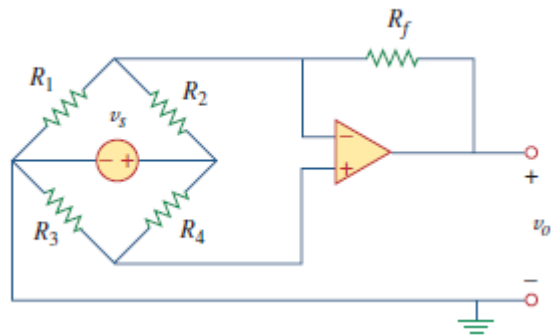


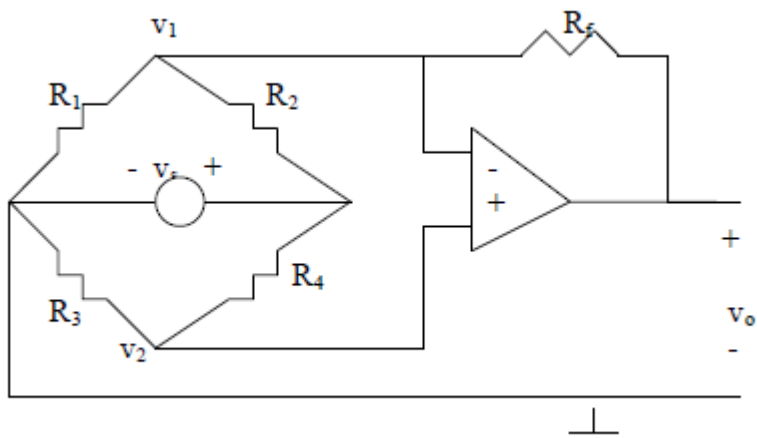Q1 In the circuit shown below, find  $k$  in the voltage transfer function  $v_o = kv_s$ .



Solution



Method-1

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_f}\right) V_1 - \frac{V_s}{R_2} = \frac{V_o}{R_f} \quad \text{--- (1)}$$

$$V_1 = \frac{R_3}{R_3 + R_4} V_s \quad \text{--- (2)}$$

putting (2) in (1)

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_f}\right) \left(\frac{R_3}{R_3 + R_4}\right) V_s - \frac{V_s}{R_2} = \frac{V_o}{R_f}$$

$$\Rightarrow V_s \left[ \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_f}\right) \left(\frac{R_3}{R_3 + R_4}\right) - \frac{1}{R_2} \right] = \frac{V_o}{R_f}$$

$$\Rightarrow K = \frac{V_o}{V_s} = R_f \left[ \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_f}\right) \left(\frac{R_3}{R_3 + R_4}\right) - \frac{1}{R_2} \right]$$

Method-2

from (1),

$$V_1 \left(\frac{1}{R_1} + \frac{1}{R_f}\right) + \frac{V_1}{R_2} - \frac{V_s}{R_2} = \frac{V_o}{R_f}$$

from (2)

$$V_s = \left(1 + \frac{R_4}{R_3}\right) V_1$$

$$\Rightarrow V_1 \left(\frac{1}{R_1} + \frac{1}{R_f}\right) + \frac{V_1}{R_2} - \frac{1}{R_2} \left(1 + \frac{R_4}{R_3}\right) V_1 = \frac{V_o}{R_f}$$

$$\Rightarrow V_1 \left(\frac{1}{R_1} + \frac{1}{R_f}\right) + \cancel{\frac{V_1}{R_2}} - \cancel{\frac{V_1}{R_2}} - \frac{V_1 R_4}{R_2 R_3} = \frac{V_o}{R_f}$$


$$\Rightarrow V_1 \left[ \frac{1}{R_1} + \frac{1}{R_f} - \frac{R_4}{R_2 R_3} \right] = \frac{V_o}{R_f}$$

$$\Rightarrow \frac{V_1}{R_3} \left[ \frac{R_3}{R_1} + \frac{R_3}{R_f} - \frac{R_4}{R_2} \right] = \frac{V_o}{R_f}$$

$$\Rightarrow \frac{V_s}{R_3 + R_4} \left[ \frac{R_3}{R_1} + \frac{R_3}{R_f} - \frac{R_4}{R_2} \right] = \frac{V_o}{R_f} \quad \text{[from eq. (2)]}$$

$$\Rightarrow K = \frac{V_o}{V_s} = \frac{R_f}{(R_3 + R_4)} \left[ \frac{R_3}{R_1} + \frac{R_3}{R_f} - \frac{R_4}{R_2} \right]$$

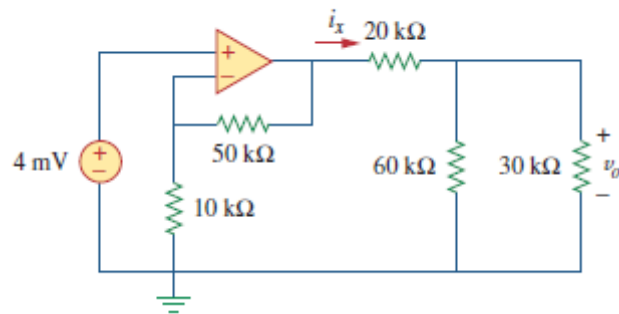Q2 Calculate  $i_x$  and  $v_o$  in the circuit of Figure shown below. Find the power dissipated by the 60-k resistor.



Solution:

Let  $v_x$  = the voltage at the output of the op amp. The given circuit is a non-inverting amplifier.

$$v_x = \left(1 + \frac{50}{10}\right)(4 \text{ mV}) = 24 \text{ mV}$$

$$60 \parallel 30 = 20 \text{ k}\Omega$$


By voltage division,

$$v_o = \frac{20}{20 + 20} v_x = \frac{v_x}{2} = 12 \text{ mV}$$

$$i_x = \frac{v_x}{(20 + 20) \text{ k}} = \frac{24 \text{ mV}}{40 \text{ k}} = 600 \text{ nA}$$

$$p = \frac{v_o^2}{R} = \frac{144 \times 10^{-6}}{60 \times 10^3} = 2.4 \text{ nW}$$

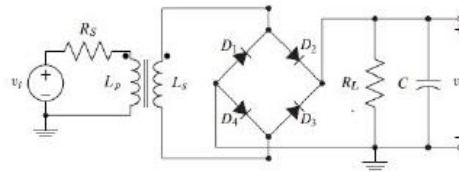3. Consider the full-wave rectifier circuit as shown below with  $C = 47\mu\text{F}$  and transformer winding ratio of 14:1. If the input voltage is 120 VAC (RMS) at 60 Hz, what is the load resistor value for a peak-to-peak ripple less than 0.5 V? What is the output DC voltage? Assume ideal diode.



Soln:

Q.3

Solution

Given transformer ratio 14:1, voltage across secondary is,

$$V_m = \frac{120\sqrt{2}}{14} = 12.1\text{V}$$

As peak-to-peak ripple voltage is given,

$$V_r = \frac{V_m}{2f_0RC} = \frac{12.1}{2 \times 60 \times R \times (47 \times 10^{-6})} < 0.5$$

$$R > 4.29\text{K}\Omega$$

So, load resistance should be greater than 4.29


If exact value calculated, then Output Dc voltage  $V_{dc} = V_m - V_r(pp)/2$   
 $= 12.1 - 0.25 = 11.85$

If range, then (11.85, 12.1] for  $V_r < 0.5$

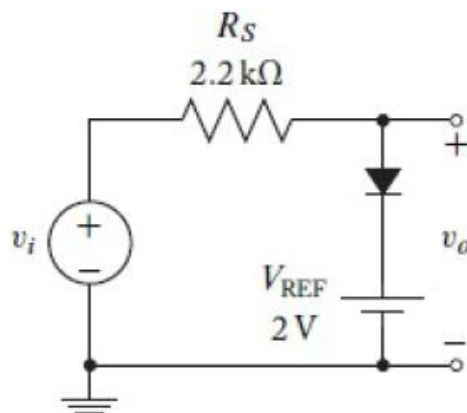4. For the clipping circuit shown, find the output waveform  $v_o$  for the input voltage,

$$v_i = 5 \sin \omega_o t.$$

The diode has the following characteristics:  $r_d = 15 \, \Omega$ ;  $V_d = 0.7 \, \text{V}$ ; and  $r_r \approx \infty$




**Solution #1:**

Since  $R_S \gg r_d$ , the simplified output voltage result from Table 2.1 can be constructed. That is,

$$\begin{aligned} v_o &= V_d + V_{ref}, & v_i &> V_d + V_{ref} \\ v_o &= v_i, & v_i &\leq V_d + V_{ref}. \end{aligned}$$

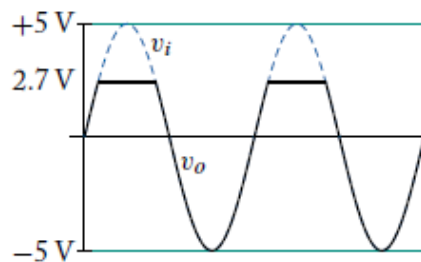
Therefore, when  $v_i > 2.7 \, \text{V}$ ,  $v_o = 2.7 \, \text{V}$  and when  $v_i < 2.7 \, \text{V}$ ,  $v_o = 5 \sin \omega_o t$ . The output waveform is shown in Figure 2.15.



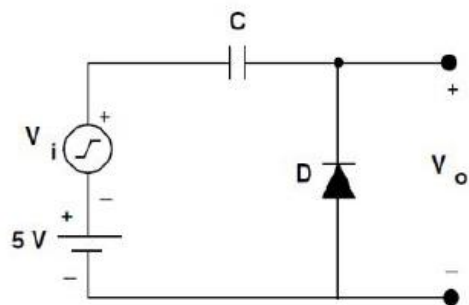5. For the circuit shown in the figure, draw the waveform of output voltage  $V_o$  for the input voltage,

$$v_i = 5 \sin \omega_o t.$$


Assume ideal diode D and lossless capacitor C.



Soln:

Explanation 2.5 marks

**Input waveform**

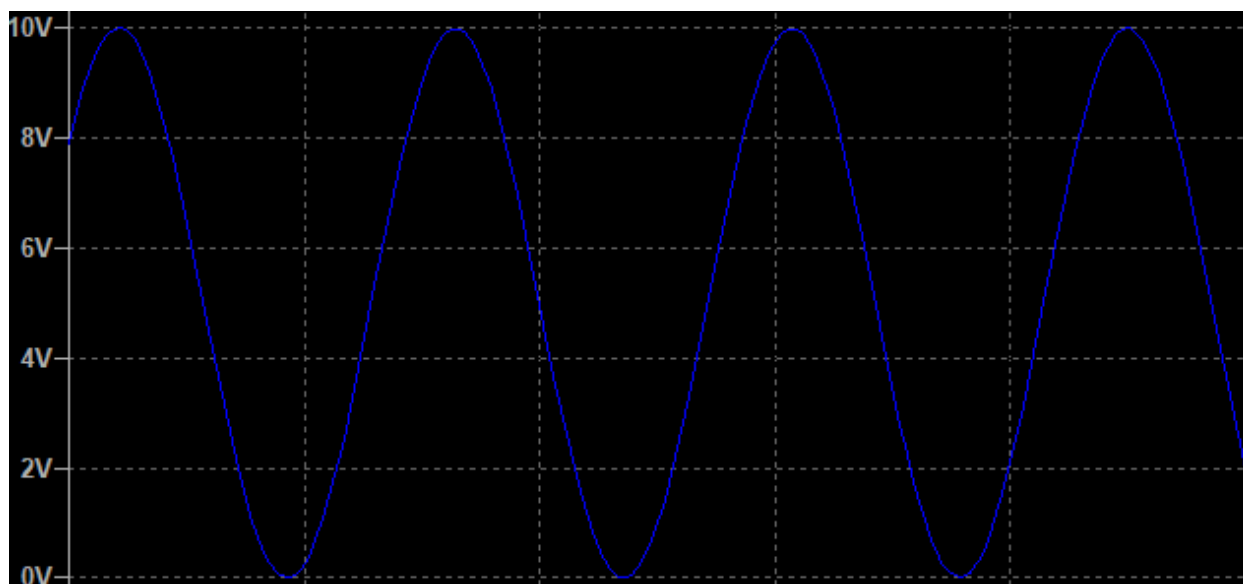

Output wave form

If cut in voltage of diode is neglected the input waveform = output waveform.

