

### SOLUTION 1


For  $t < 0$ : (1)  $L_1, L_2$  are short, and (2) no current flows through any of the 4 resistors,  $\Rightarrow$

$$i_1(0^-) = -8 \text{ A}, i_2(0^-) = -4 \text{ A}, i_3(0^-) = 0,$$

$$w_1(0^-) = (5 \text{ H})(8 \text{ A})^2 / 2 = 160 \text{ J}, w_2(0^-) = (20)(4)^2 / 2 = 160 \text{ J}.$$

For  $t > 0$ , switch is open, the initial energy stored in the 2 inductors is dissipated via the 4 resistors.


The **equivalent circuit** becomes:

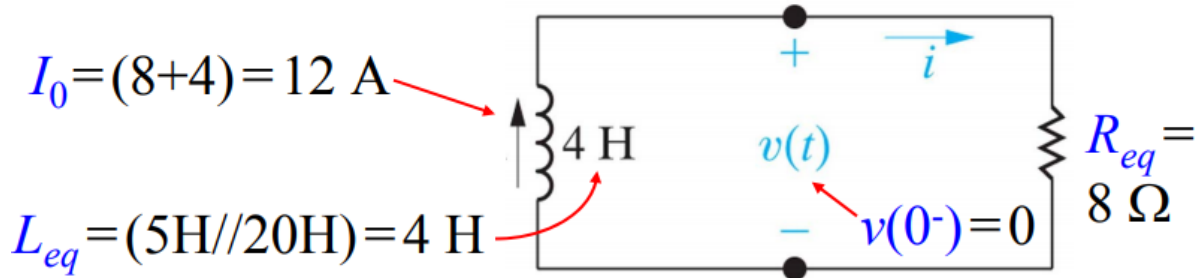

The solutions to  $i(t)$ ,  $v(t)$  are:

$$\tau = \frac{L_{eq}}{R_{eq}} = \frac{4}{8} = 0.5 \text{ s}, \Rightarrow \begin{cases} i(t) = I_0 e^{-(t/\tau)} = 12e^{-2t} \text{ A}, \\ v(t) = Ri(t) = 96e^{-2t} \text{ V}. \end{cases}$$

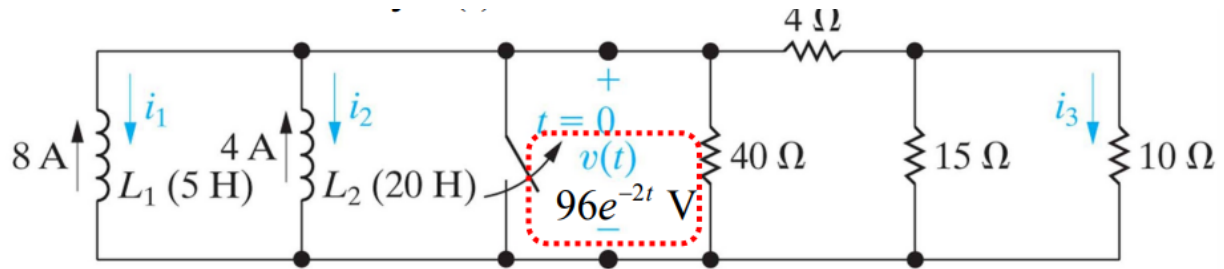The two inductor currents  $i_1(t)$ ,  $i_2(t)$  can be calculated by  $v(t)$ :



$$i_1(t) = i_1(0) + \frac{1}{L_1} \int_0^t v(t') dt' = -8 + \frac{1}{5} \int_0^t 96e^{-2t'} dt' = 1.6 - 9.6e^{-2t} \text{ A.}$$


$$i_2(t) = i_2(0) + \frac{1}{L_2} \int_0^t v(t') dt' = -4 + \frac{1}{20} \int_0^t 96e^{-2t'} dt' = -1.6 - 2.4e^{-2t} \text{ A.}$$

The **energies** stored in the two inductors are:

$$w_1(t \rightarrow \infty) = \frac{1}{2} (5 \text{ H})(1.6 \text{ A})^2 = 6.4 \text{ J,}$$

$$w_2(t \rightarrow \infty) = \frac{1}{2} (20)(-1.6)^2 = 25.6 \text{ J,}$$

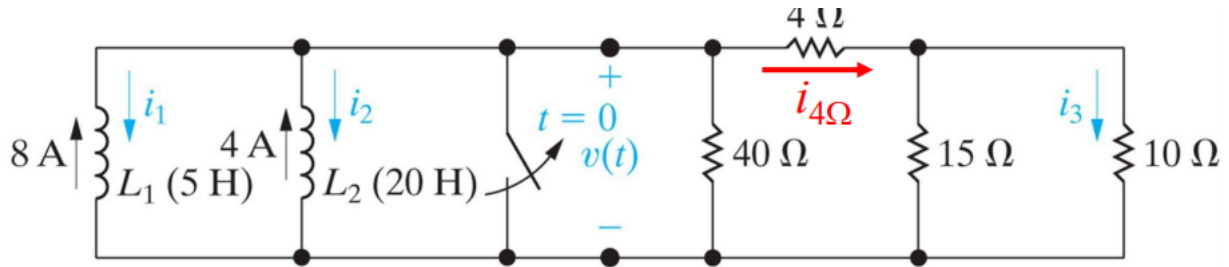By current division,  $i_3(t) = 0.6i_{4\Omega}(t)$ , while  $i_{4\Omega}(t)$  can be calculated by  $v(t)$ :



$$i_{4\Omega}(t) = \frac{v(t)}{4\Omega + (15\Omega // 10\Omega)} = \frac{96e^{-2t}}{10} = 9.6e^{-2t} \text{ A.}$$

$$\Rightarrow i_3(t) = \frac{3}{5}i_{4\Omega}(t) = 5.76e^{-2t} \text{ A.}$$

## SOLUTION 2

We find  $R_N$  in the same way we find  $R_{Th}$  in the Thevenin equivalent circuit. Set the independent sources equal to zero. This leads to the circuit in Fig. 4.40(a), from which we find  $R_N$ . Thus,




$$R_N = 5 \parallel (8 + 4 + 8) = 5 \parallel 20 = \frac{20 \times 5}{25} = 4 \Omega$$

To find  $I_N$ , we short-circuit terminals  $a$  and  $b$ , as shown in Fig. 4.40(b). We ignore the  $5\text{-}\Omega$  resistor because it has been short-circuited. Applying mesh analysis, we obtain

$$i_1 = 2 \text{ A}, \quad 20i_2 - 4i_1 - 12 = 0$$

From these equations, we obtain

$$i_2 = 1 \text{ A} = i_{sc} = I_N$$

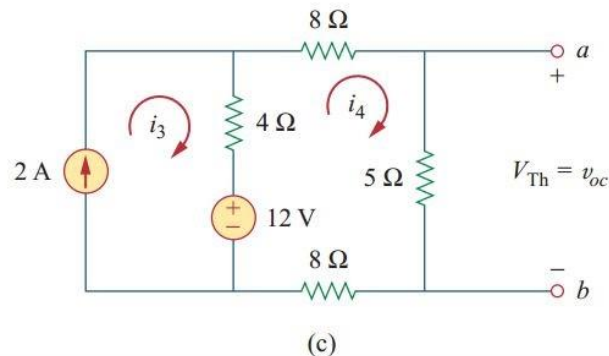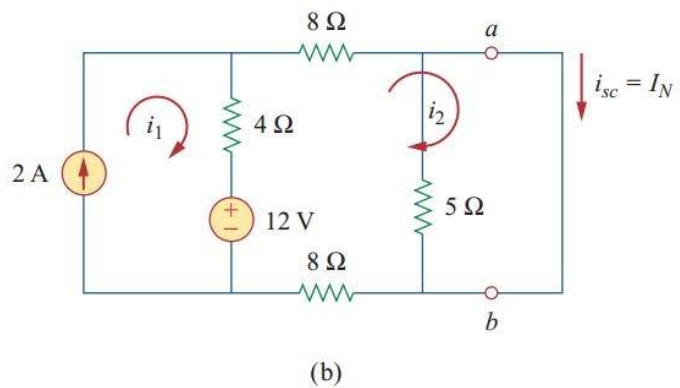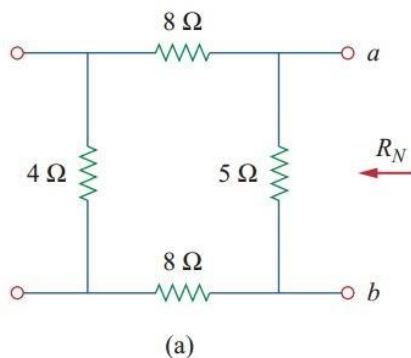

Alternatively, we may determine  $I_N$  from  $V_{Th}/R_{Th}$ . We obtain  $V_{Th}$  as the open-circuit voltage across terminals  $a$  and  $b$  in Fig. 4.40(c). Using mesh analysis, we obtain

$$i_3 = 2 \text{ A}$$

$$25i_4 - 4i_3 - 12 = 0 \quad \Rightarrow \quad i_4 = 0.8 \text{ A}$$


and

$$v_{oc} = V_{Th} = 5i_4 = 4 \text{ V}$$

Hence,

$$I_N = \frac{V_{Th}}{R_{Th}} = \frac{4}{4} = 1 \text{ A}$$


as obtained previously. This also serves to confirm Eq. (4.12c) that  $R_{Th} = v_{oc}/i_{sc} = 4/1 = 4 \Omega$ . Thus, the Norton equivalent circuit is as shown in Fig. 4.41.

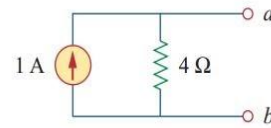

**Figure 4.41**

Norton equivalent of the circuit in Fig. 4.39.

### Solution 3

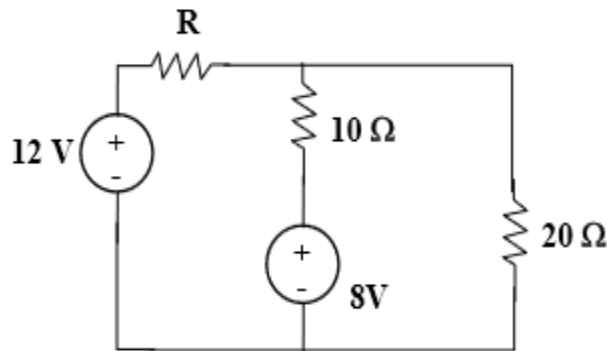

Removing the 10 ohm resistor and solving for the Thevenin Circuit results in:

$$R_{Th} = (R \times 20 / (R + 20)) \text{ and } V_{oc} = V_{Th} = 12 \times (20 / (R + 20)) + (-8)$$

As  $R$  goes to zero,  $R_{Th}$  goes to zero and  $V_{Th}$  goes to 4 volts, which produces the maximum power delivered to the 10-ohm resistor.

$$P = v_i = v^2 / R = 4 \times 4 / 10 = 1.6 \text{ watts}$$

Notice that if  $R = 20$  ohms which gives an  $R_{Th} = 10$  ohms, then  $V_{Th}$  becomes -2 volts and the power delivered to the load becomes 0.1 watts, much less than the 1.6 watts.

#### Solution 4

$$(a) \quad \tau = RC = \frac{1}{4}$$

$$-i = C \frac{dv}{dt}$$

$$-0.2 e^{-4t} = C(10)(-4)e^{-4t} \longrightarrow C = \underline{\mathbf{5 \text{ mF}}}$$

$$R = \frac{1}{4C} = \underline{\mathbf{50 \, \Omega}}$$

$$(b) \quad \tau = RC = \frac{1}{4} = \underline{\mathbf{0.25 \text{ s}}}$$

$$(c) \quad w_c(0) = \frac{1}{2} C V_0^2 = \frac{1}{2} (5 \times 10^{-3})(100) = \underline{\mathbf{250 \text{ mJ}}}$$

$$(d) \quad w_R = \frac{1}{2} \times \frac{1}{2} C V_0^2 = \frac{1}{2} C V_0^2 (1 - e^{-2t_0/\tau})$$


$$0.5 = 1 - e^{-8t_0} \longrightarrow e^{-8t_0} = \frac{1}{2}$$

$$\text{or} \quad e^{8t_0} = 2$$

$$t_0 = \frac{1}{8} \ln(2) = \underline{\mathbf{86.6 \text{ ms}}}$$

### Solution 5

Using source transform

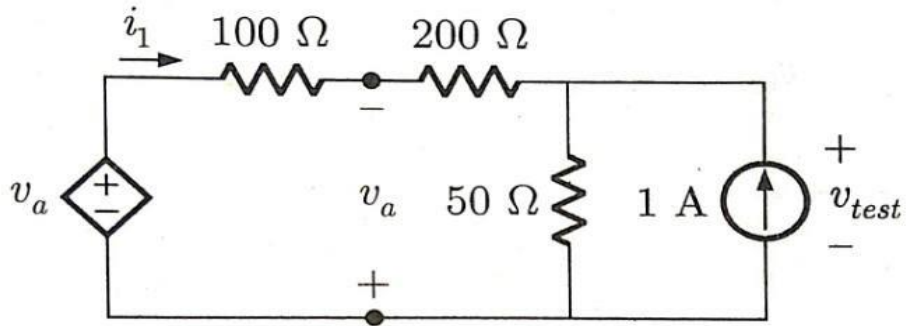

$$v_a = 100i_1 + 200i_1 + 50(i_1 + 1)$$

$$\Rightarrow \begin{aligned} v_a &= 100i_1 - v_a \\ v_a &= 50i_1 \end{aligned}$$

$$50i_1 = 300i_1 + 50i_1 + 50$$

$$\Rightarrow i_1 = -\frac{1}{6} \text{ A}$$

$$v_{test} = 50\left(1 - \frac{1}{6}\right) = \frac{125}{3} \Omega$$